



NSF NRT-InFEWS: Indigenous Food, Energy, and
Water Security and Sovereignty
Presents:



Food, Energy and Water (FEWS) Learning Modules

June 2021





Electrical Design Basics and Considerations

Presented by Frances Willberg

Please have a calculator on hand
(phone, computer, handheld, etc)





Voltage



Voltage (Volts) is a quantity that measures electrical potential in an electrical system. The symbol (V) is used to represent voltage.

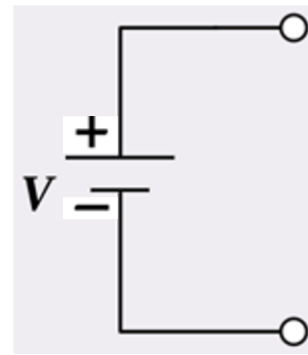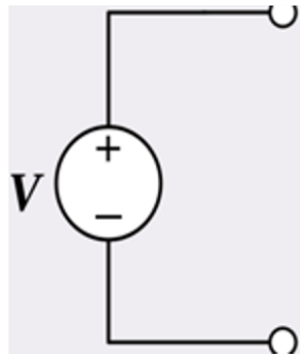Batteries and energy sources (PV) are viewed as voltage sources.







Current



Current (Amps, A) represents the rate of electron charge flow. The symbol (I) is used to represent current.

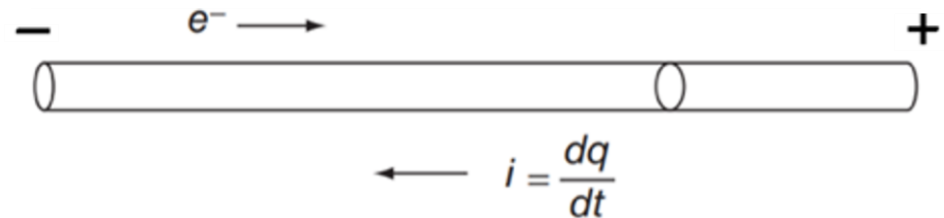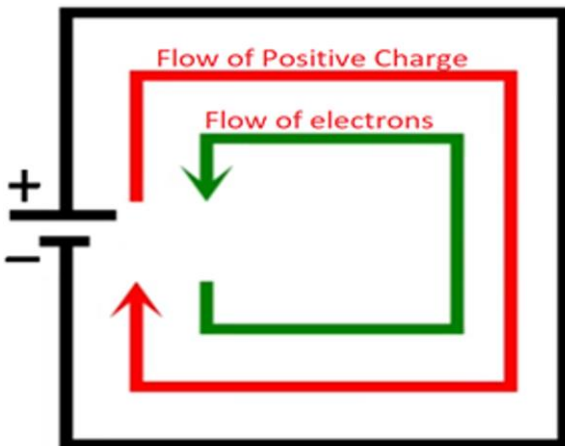By convention, negative charges moving in one direction constitutes a positive current flow in the opposite direction





Resistance




Resistance (Ohms, Ω) is the opposition to the flow of current. The symbol (R) is used to represent resistance.

* Ohm's Law:

$$V = IR$$

$$I = \frac{V}{R}$$

$$R = \frac{V}{I}$$

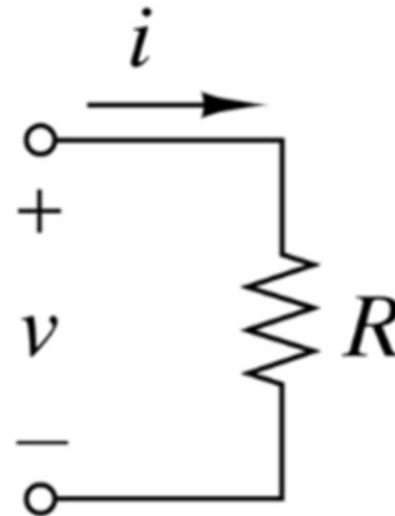



Ohm's Law Example




Solve for the unknown quantity

Solution: *Ohm's Law: $V = IR$*

V = Voltage (V)

I = Current (A)

R = Resistance (Ω)

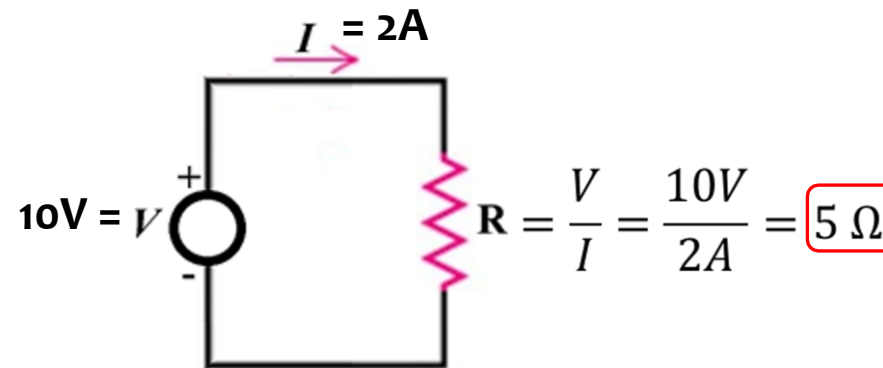



Power



Power (Watts) is the measure of energy per unit time.

$$P = V * I = (\text{voltage}) * (\text{current})$$
$$= \frac{V^2}{R} = I^2 R$$

V = Voltage (V)
I = Current (A)
R = Resistance (Ω)




Power Example

Solve for the power absorbed by the resistor

Solution: *Power:* $P = IV = I^2R$

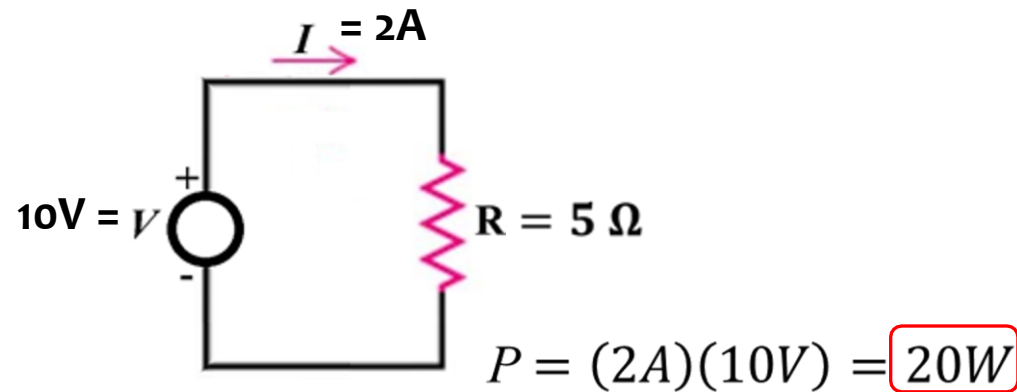V = Voltage (V)
I = Current (A)
R = Resistance (Ω)
P = Power (P)





Energy



Energy is the power consumed over a period of time (seconds or hours).

$$\text{Energy} = \text{Power} \times \text{time} = \text{Watts} \times \text{sec}$$

e.g. 10Ws, 5 kWh (5000Wh)

$$E/t = P$$
$$E = P * t = IVt$$

V = Voltage (V)
I = Current (A)
t = Time (hr/sec)



Energy Example



Solve for the energy absorbed by a 500W heater over 3 hours

$$P = 500\text{W}$$

$$t = 3 \text{ hours}$$

$$\textit{Energy: } E = Pt = IVt$$

Solution:

$$\begin{aligned} E &= Pt = (500\text{W})(3\text{hr}) \\ &= \boxed{1500\text{Whr} = 1.5 \text{kWhr}} \end{aligned}$$



V = Voltage (V)
I = Current (A)
R = Resistance (Ω)
P = Power (P)
E = Energy (Whr)



Equations & Conversions



- * $\text{Power} = V \times I = I^2R = \text{Energy} \div \text{time}$
1000 Watts = 1 kiloWatt (kW)
1 Watt = 1 Volt x 1 Amp
- * $\text{Voltage} = I \times R$
1 Volt = 1000 milliVolts (mV)
- * $\text{Current} = V/R$
1 Amp = 1000 milliAmps (mA)
- * $\text{Resistance} = V / I$
1 Ohm = 1 Volt \div 1 Amp
- * $\text{Energy} = P \times t$
1 kiloWatt hour (kWhr) = 1000 Watt hours (Wh)



Units and Dimensions

1 kilo = 1,000x
1 mega = 1,000,000x
1 giga = 1,000,000,000x
1 tera = 1,000,000,000,000x

- **Power** = rate of energy expenditure (Watts, kilowatts, ...)
- Electrical power = voltage x current = 1 Watt = 1 Volt x 1 Amp
- 1 horsepower = 746 Watts

- **Energy** = power use over time (watt-hour, BTU, Joule, Calorie)
- 1,000 BTU's = 293 W-hr
- 1,000 calories = 1.16 W-hr
- 1,000 Joules = 1,000 Newton-meter = 0.278 W-hr
- 1 W-hr = 2.25×10^{22} electron volts




PV as a Power Source:



PV circuit representation:

- * PV is used as a voltage source

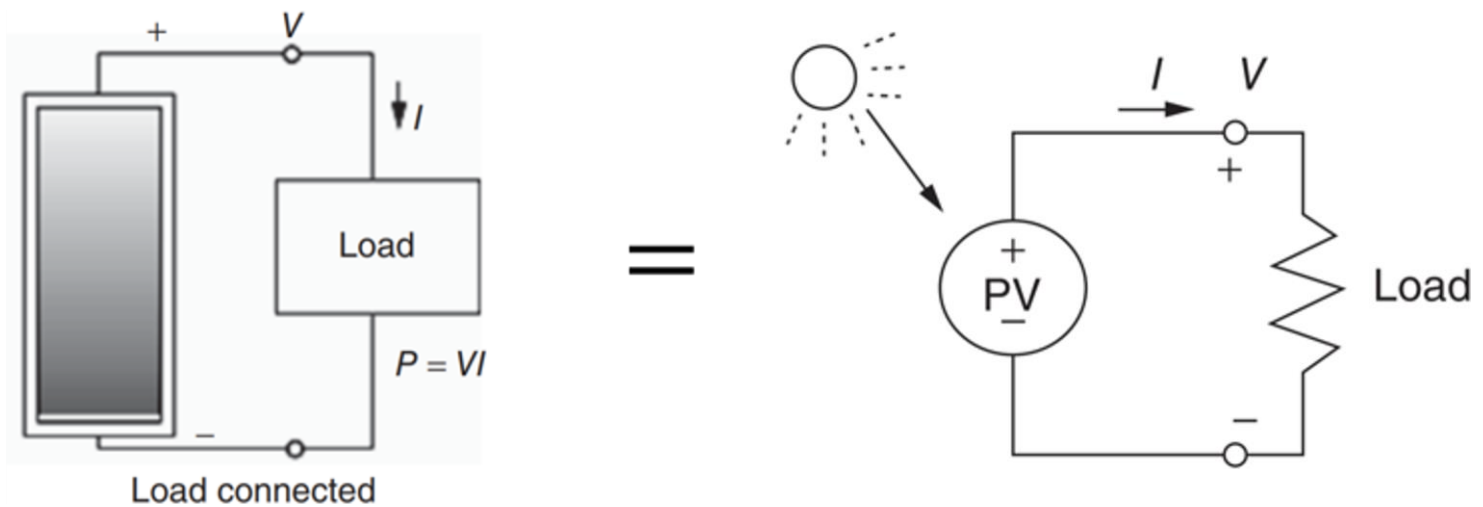







PV as a Power Source:



Two conditions of interest

- * Short-circuit current, I_{SC}
 - * Terminals are shorted, current is measured
- * Open-circuit voltage, V_{OC}
 - * Terminals are open, voltage is measured

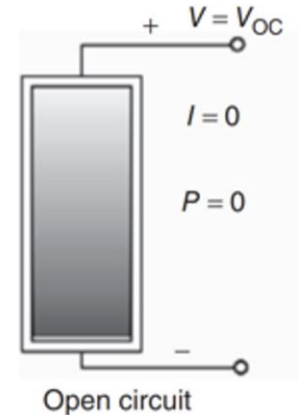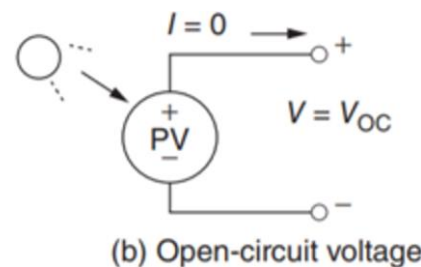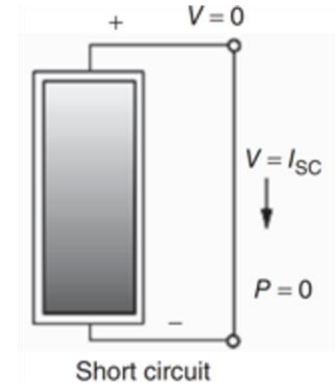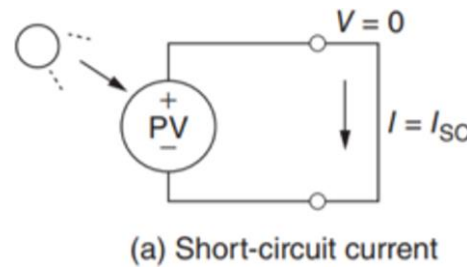




PV I-V Relationship:



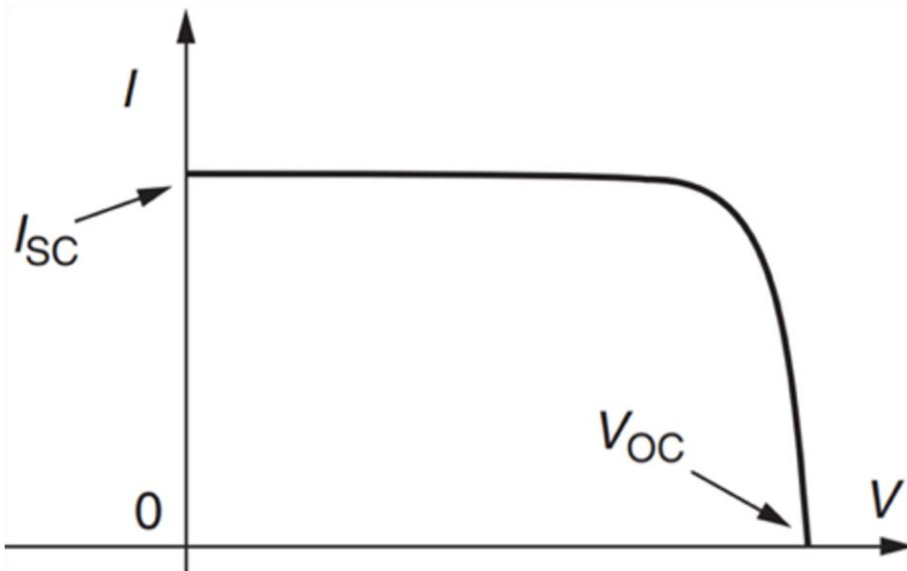V.curve shows the relationship between voltage and current for a PV cell.



- Remember that Power is equal to Voltage x Current ($P = IV$).
- Maximum Power is the point at which the product of voltage and current is maximum.
- Notice that current is maximum at I_{sc} but voltage is zero.
- Likewise, the voltage is maximum at V_{oc} but current is zero.



PV Sticker Information



Trinasolar
Smart Energy Together

TSM-305PC14 Made in China

Maximum Power (P_{max})	305W $^{+3\%}_0$
Maximum Power Voltage (V_{mp})	36.6V
Maximum Power Current (I_{mp})	8.33A
Open Circuit Voltage (V_{oc})	45.5V
Short Circuit Current (I_{sc})	8.81A
Maximum System Voltage	DC1000V
Maximum Series Fuse	15A
Module Application	Class A

For field connections, use minimum 4mm² copper wires insulated for a minimum 90°C


Electrical Rating At STC
AM=1.5 IRRADIANCE=1000W/m² Temp.=25°C

EU-26 WEEE Compliant Electrical Hazard

This module produces electricity when exposed to light.
Follow all applicable electrical safety precautions.

Changzhou Trina Solar Energy Co., Ltd.
www.trinasolar.com

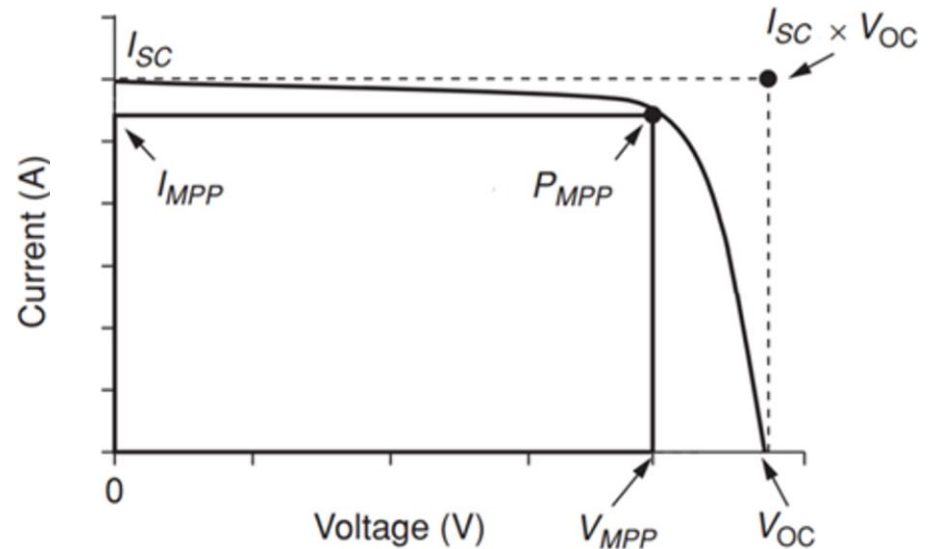Remember that $P_{MPP} = I_{MPP} \times V_{MPP}$







PV Panels in Series:



For PV modules in series,

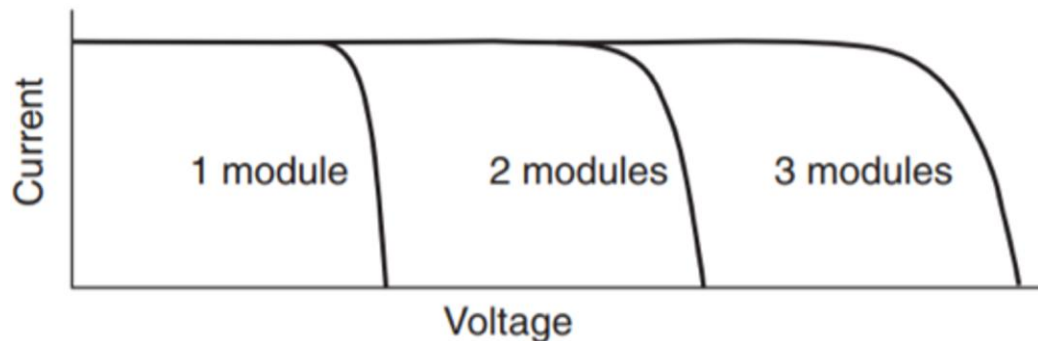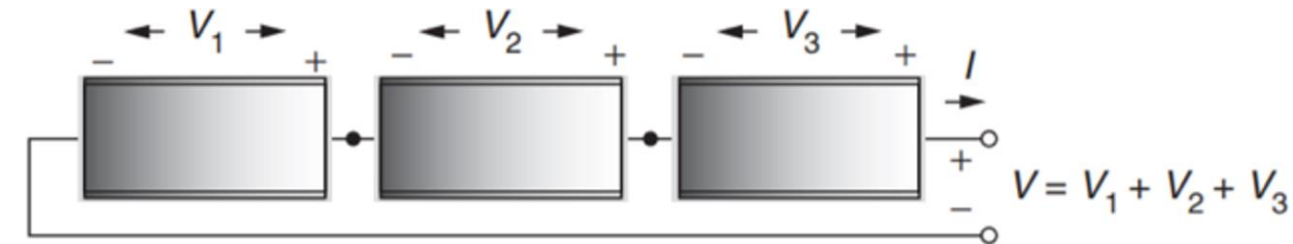- * Voltage adds
- * Current remains constant







PV Panels in Parallel:



For PV modules in parallel,

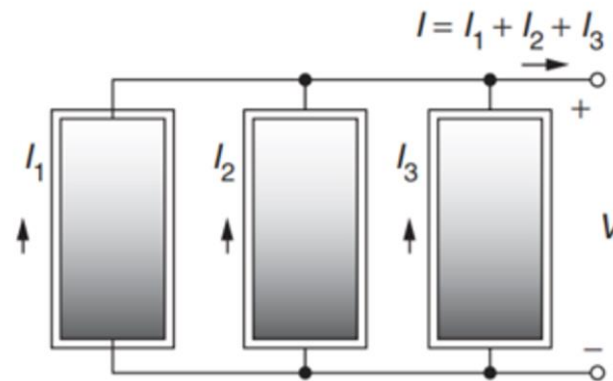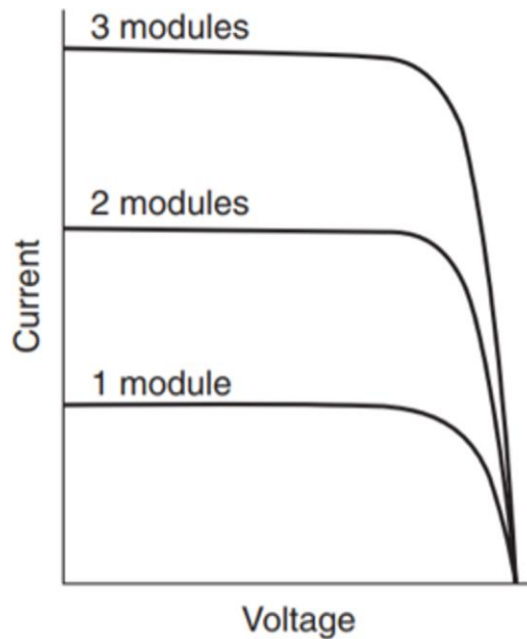- * Current adds
- * Voltage remains constant





Useful Information



- * Power = $V \times I = I^2R = \text{Energy} \div \text{time}$
1000 Watts = 1 kiloWatt (kW) 1
Watt = 1 Volt x 1 Amp
- * Voltage = $I \times R$
1 Volt = 1000 milliVolts (mV)
- * Current = V/R
1 Amp = 1000 milliAmps (mA)
- * Resistance = V / I
1 Ohm = 1 Volt \div 1 Amp
- * Energy = $P \times t$
1 kiloWatt hour (kWh) = 1000 Watt hours (Wh)

PV panels in series:

- Current remains constant
- Voltages add

PV panels in parallel:

- Voltage remains constant
- Currents add





PV Configurations Example



Suppose each PV panel has the following:

$I_{sc} = 2A$, $V_{oc} = 10V$. What should the total I_{sc} and V_{oc} be for the following array configurations?

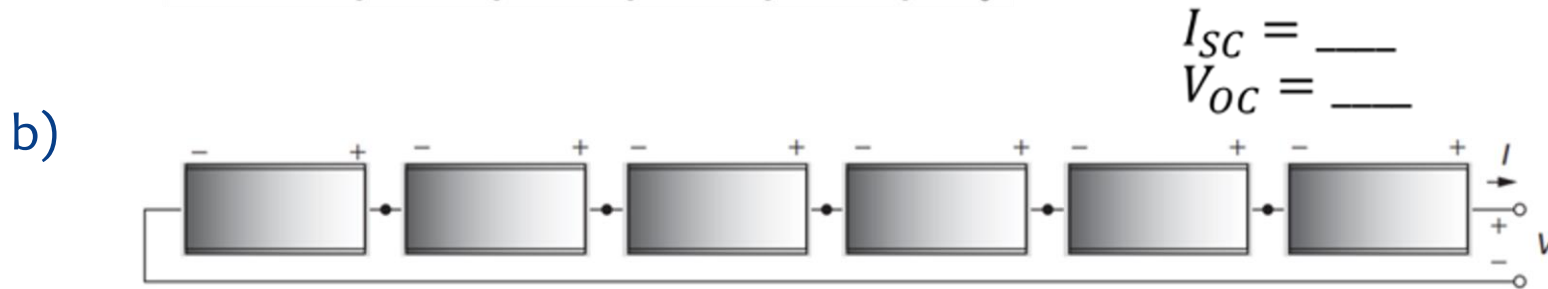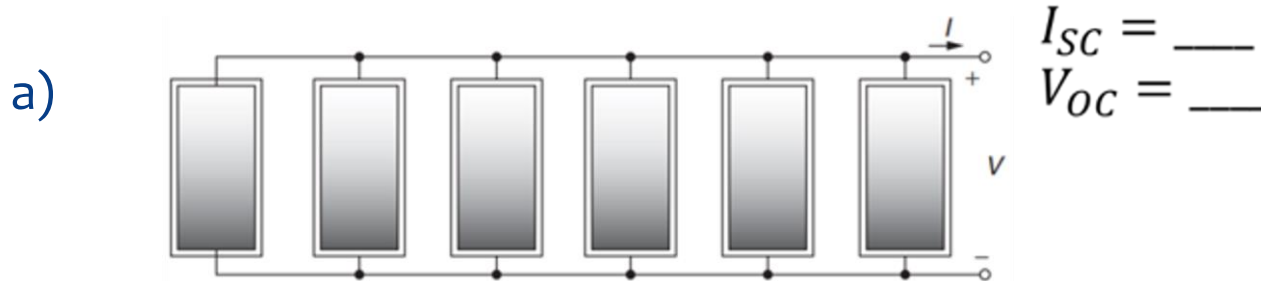Remember that voltage adds in series and current adds in parallel





PV Configurations Example




Suppose each PV panel has the following:


$I_{SC} = 2A$, $V_{OC} = 10V$. What should the total I_{SC} and V_{OC} be for the following array configurations?

Remember that voltage adds in series and current adds in parallel

Solution:

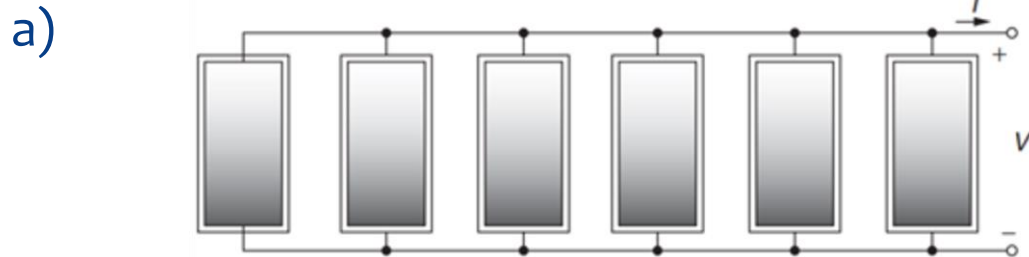
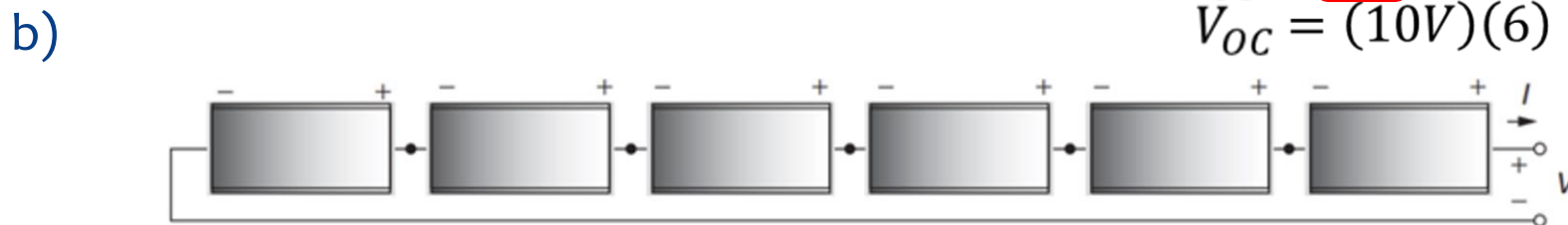
$$I_{SC} = (2A)(6) = 12A$$
$$V_{OC} = 10V$$



$$I_{SC} = 2A$$
$$V_{OC} = (10V)(6) = 60V$$



PV Configurations Example




Suppose each PV panel has the following:

$I_{SC} = 2A$, $V_{OC} = 10V$. What should the total I_{SC} and V_{OC} be for the following array configurations?

Remember that voltage adds in series and current adds in parallel

Solution:

c)

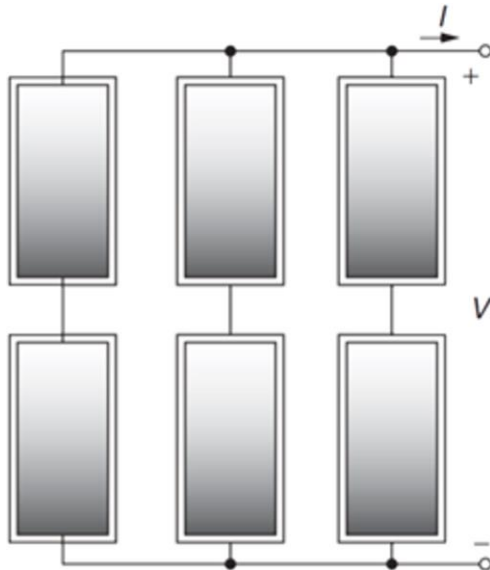

Add panels in series first, then add strings of panels in parallel

$$I_{SC} = (2A)(3) = 6A$$
$$V_{OC} = (10V)(2) = 20V$$




Direct Current



Direct Current (DC) is when charge flows at a steady rate in **one direction** only

Batteries, PV, Wind provide DC current.

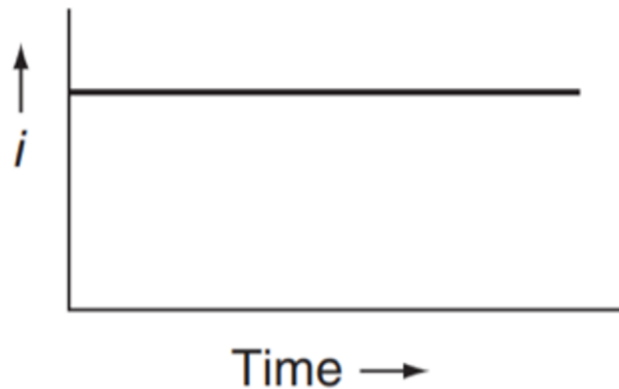





Alternating Current



Alternating Current (AC) is when charge flows back and forth sinusoidally.

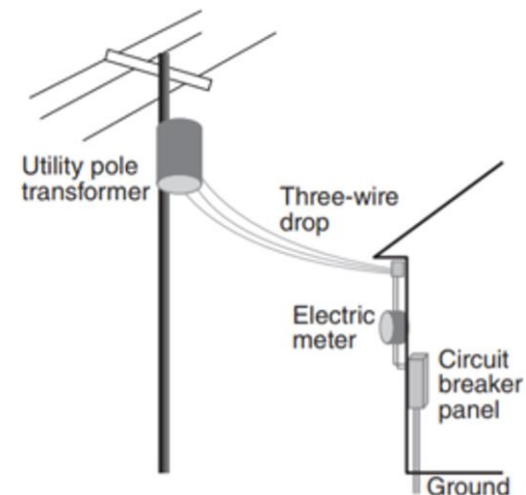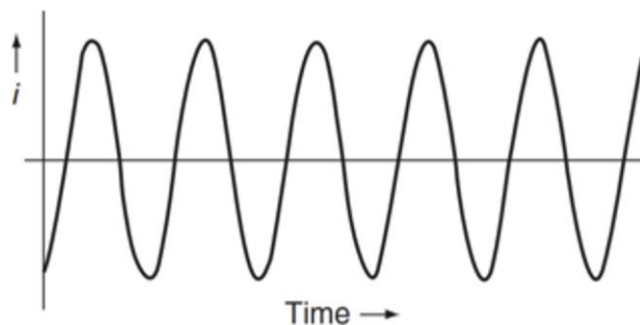- * AC electricity in the US delivered by utility has a frequency (the rate at which the direction changes) of 60 cycles/s or 60 Hz
- * Inverters can be used convert from DC to AC





Digital Multimeter



AC/DC Toggle Button

Control Dial

Positive Probe (Red)

Amp (A) input

Miliamp (mA) / microamp (μ A) input

Alternating Current (AC): ~

Direct Current (DC): =

Display

Negative probe (Black)

Voltage/resistance/diode measurement input

COM (negative) input



Digital Multimeter PV Measurement Demonstration





Power Consumption



When computing the impact of any appliance on total power consumption, it is very important to look not just at the rate of power use (in watts per hour), but also at the number of hours per day (or year) of typical use.

Example:

- A laptop computer uses 15-60 watts per hour, 10 hours per day
= 150 to 600 Watts of energy consumed each day
- A toaster oven uses 1200 watts per hour, 5 minutes per day
(1200 W/hr) ÷ (60 minutes/hour) = 20 Watts per minute
(20 W/min) x (5 minutes) = 100 W per day



EnergyStar Appliances



EnergyStar appliances are held to strict standards by the US Environmental Protection Agency (EPA) to be more energy efficient than their conventional counterparts.

They can be more expensive upfront, but the energy savings they deliver can result in significant cost savings over the life of the appliance.





Lists key features of the appliance you're looking at and the similar models that make up the cost range below.

U.S. Government Federal law prohibits removal of this label before consumer purchase.

ENERGYGUIDE

Refrigerator-Freezer
 • Automatic Defrost
 • Side-Mounted Freezer
 • Through-the-Door Ice

XYZ Corporation
 Model ABC-L
 Capacity: 23 Cubic Feet

Estimated Yearly Operating Cost

\$67

Cost Range of Similar Models: \$57 to \$74

630 kWh
 Estimated Yearly Electricity Use

Your cost will depend on your utility rates and use.

- Cost range based only on models of similar capacity with automatic defrost, side-mounted freezer, and through-the-door ice.
- Estimated operating cost based on a 2007 national average electricity cost of 10.65 cents per kWh.
- For more information, visit www.ftc.gov/appliances.

The maker, model, and size tell you exactly what product this label describes.

What you might pay to run the appliance for a year, based on its electricity use and the national average cost of energy. The cost appears on labels for all models and brands, so you can compare energy use just like you would price or other features.

The cost range helps you compare the energy use of different models by showing you the range of operating costs for models with similar features.

An estimate of how much electricity the appliance uses in a year based on typical use. Multiply this by your local electricity rate on your utility bill to better judge what your actual operating cost might be.

If you see the ENERGY STAR logo, it means the product is better for the environment because it uses less energy than standard models.

<https://www.consumer.ftc.gov/articles/007-2-shopping-home-appliances-use-energyguide-label>



Annual Energy Consumption of Common Appliances



Conventional Appliances:

- * Refrigerator: 327 kWh
- * Washing Machine: 187 kWh

EnergyStar Appliances:

- * Refrigerator: 297 kWh
- * Washing Machine: 93 kWh

No EnergyStar Rating:

- * Laptop: 175 kWh
- * Cell Phone Charger: 20 kWh
- * Microwave: 220 kWh



References

1 “*Digital Multimeter and PV Panel Demo for TCUP 2021*”, Frances Willberg, 25-May-2021. [Online]. Available:

<https://www.youtube.com/watch?v=aefBZXKdhw8>

2 “*What makes a product ENERGY STAR?*”, EnergyStar. [Online]. Available:

https://www.energystar.gov/products/what_makes_product_energy_star

3 “*How to Use the EnergyGuide Label to Shop for Home Appliances*”, Federal Trade Commission Consumer Information. [Online]. Available:

<https://www.consumer.ftc.gov/articles/how-use-energyguide-label-shop-home-appliances>



Indige-FEWSS Team



Karletta Chief

Environmental Science

Robert Arnold

Chemical & Environmental Engineering

Benedict J. Colombi

American Indian Studies

Murat Kacira

Biosystems Engineering

Vasiliki Karanikola

Chemical & Environmental Engineering

Kimberly Ogden

Chemical & Environmental Engineering

Erin L. Ratcliff

Chemical & Environmental Engineering

Valerie Shirley

Teaching, Learning and Sociocultural Studies

Kelly Simmons-Potter

Electrical & Computer Engineering; Optical Sciences

Benita Litson and Bryan Neztosie

Diné College, Land Grant Office

Cara Shopa, Program Coordinator

Torran Anderson, Outreach Coordinator



Food Module Authors



- **Dr. Murat Kacira**
Module Lead
Biosystems Engineering
- **Rebekah Waller**
Biosystems Engineering
- **Jaymus Lee**
Biosystems Engineering
- **Amy Pierce**
Biosystem Engineering
- **Alexandra Trahan**
Environmental Science
- **Ruth Pannill**
School of Natural Resources and the Environment



Energy Module Authors



- **Dr. Kelly Simmons-Potter**
Module Lead
Electrical & Computer Engineering
- Kyle Boyer
Electrical & Computer Engineering
- Manuelito Chief
Electrical & Computer Engineering
- Frances Willberg
Electrical & Computer Engineering
- Anna Rich
Material Science & Engineering
- William Borkan
Environmental Science



Water Module Authors



- **Dr. Robert Arnold**
Module Co-Lead
Chemical & Environmental Engineering
- **Dr. Karletta Chief**
Module Co-Lead
Environmental Science
- **Dr. Vasiliki Karanikola**
Module Co-Lead
Chemical & Environmental Engineering
- **Christopher Yazzie**
Chemical & Environmental Engineering
- **Marisa Gonzalez**
Chemical & Environmental Engineering
- **Sarah Abney**
Environmental Science
- **Ciara Lugo**
Chemical & Environmental Engineering
- **Ailyn Brizo**
Chemical & Environmental Engineering



Indigenizing Curriculum Contributors



- **Dr. Valerie Shirley**
Teaching, Learning and Sociocultural Studies
- **Dr. Karletta Chief**
Environmental Science
- **Torran Anderson**
Community Engagement Coordinator
- **Nikki Tulley**
Environmental Science
- **JoRee LaFrance**
Environmental Science
- **Marquel Begay**
School of Natural Resources & the Environment
- **Manuelito Chief**
Electrical & Computer Engineering
- **Christopher Yazzie**
Chemical & Environmental Engineering

The UArizona Indige-FEWSS NSF NRT would like to thank you for joining us today!

A NSF funded program in partnership with Diné College.



THE UNIVERSITY OF ARIZONA
RESEARCH, INNOVATION & IMPACT

Arizona Institutes
for Resilience

This material is based upon work supported by the National Science Foundation under Grant #DGE1735173.

Any opinions, findings, and conclusions or recommendations expressed in this material are those of the author(s) and do not necessarily reflect the views of the National Science Foundation